
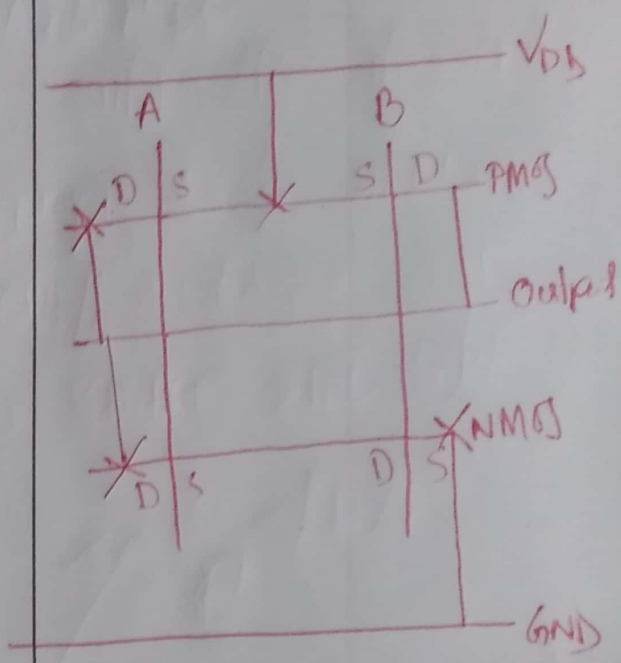


Task 01

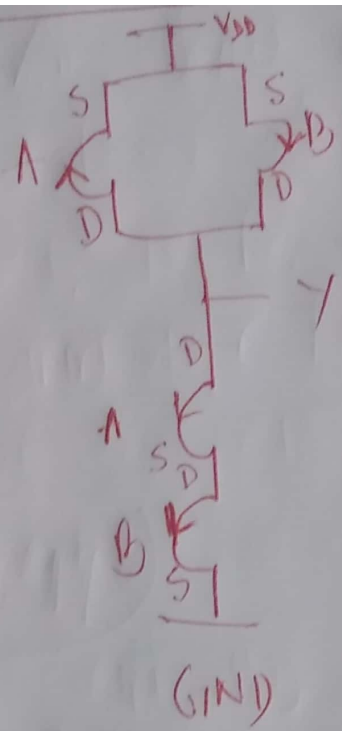

Stick Diagram

- Same Path for NMOS, PMOS
- Correctly set Source & Drain
- PMOS to GND, source & drain etc