


Question: Consider any 2-input NOR Gate: $Y = \overline{A+B}$

Task 01. Draw schematic Diagram


Task 02. Draw Euler's Path

Task 03. Draw Stick Diagram

Task 04. Implement in microwind

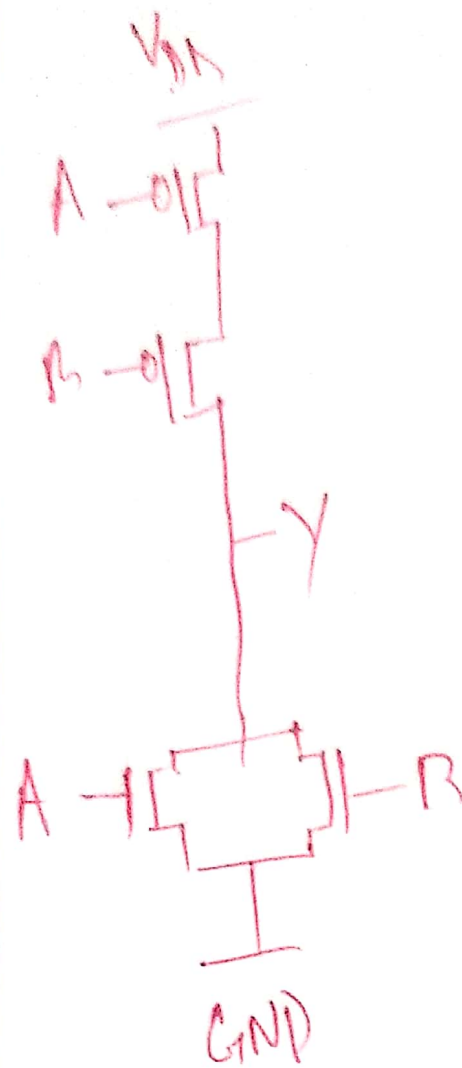


Task 01
Remember
Series
Parallel

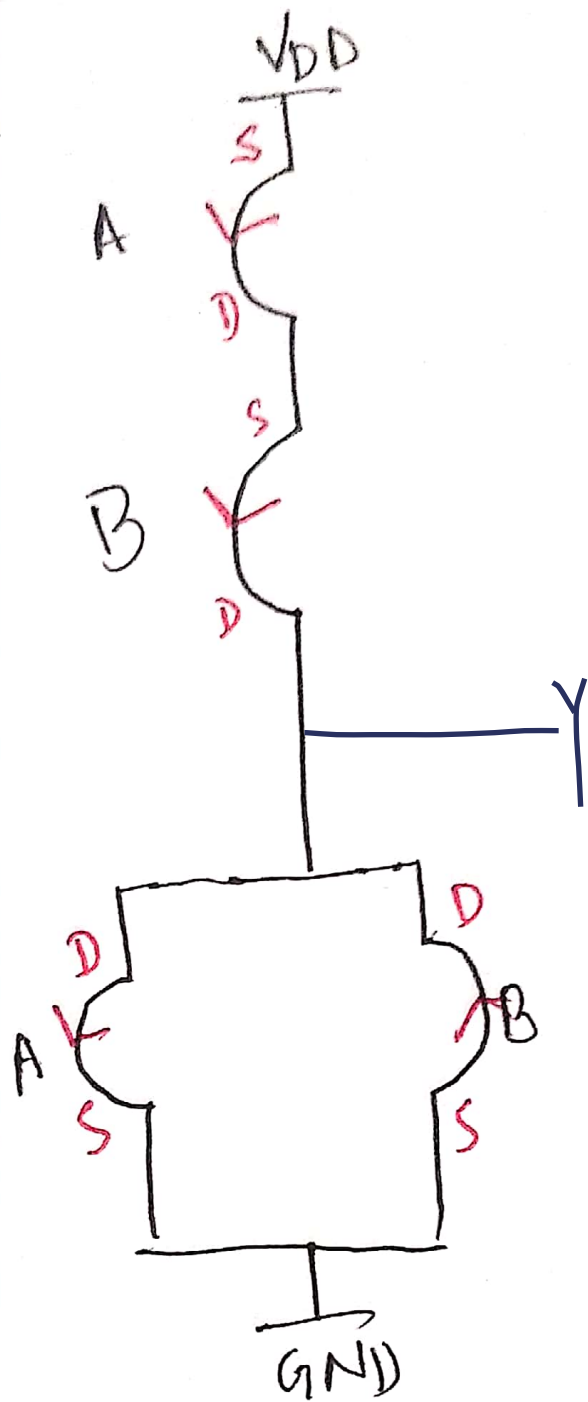

Task 02.

Path

Source-Drain

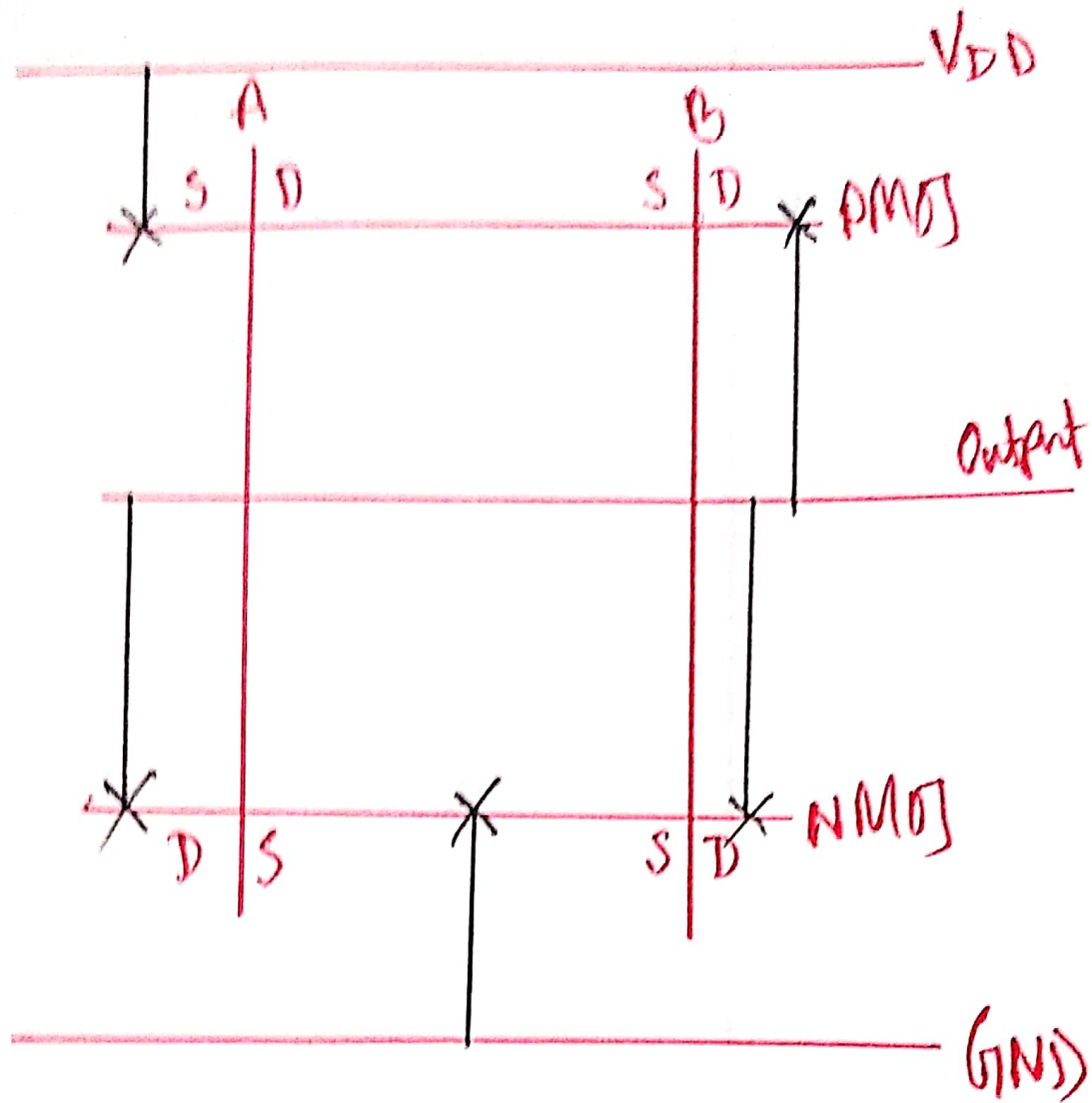

Task 03.

Remember

- connection wires

- Contacts

- Source Drain placement