

Answer to the Q. NO. 1

Given,

$$\begin{aligned} \beta &= 17201012 \\ V_{GS} &= 0.5V, 2V \\ V_t &= 1V \end{aligned}$$

We know,

$$\begin{aligned} \text{for } V_{GS} &= 0.5 \\ V_{GT} &= V_{GS} - V_t \\ &= 0.5 - 1 \\ &= -0.5 \end{aligned}$$

For saturation,

$$V_{GT} = V_{DS}$$

$$\therefore V_{DS} = -0.5V$$

$$\begin{aligned} I_{DS} &= \frac{\beta}{2} V_{GT}^2 = 0 \quad \text{As } V_{GS} < V_t \\ &= \frac{17201012}{2} (-0.5)^2 \\ &= 2150126.5 \end{aligned}$$

for,

$$V_{gs} = 2V$$


$$V_{GT} = V_{gs} - V_T$$

$$= 2 - 1$$

$$= 1 = V_{ds}$$

$$\therefore I_{ds} = \frac{17201012}{2} \times (1)^2$$

$$= 8600506$$

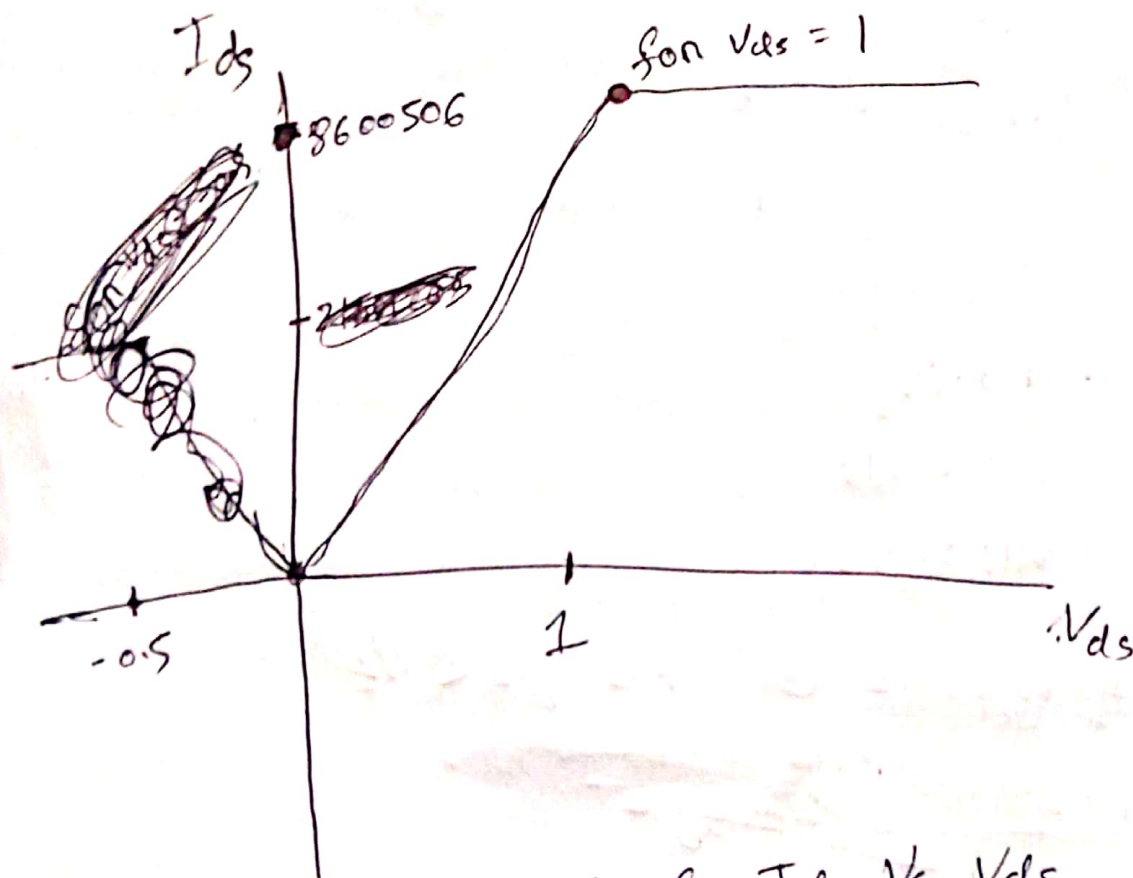

Fig(1): Plot of I_{ds} Vs. V_{ds}

Answer to the Q.No.2

Fig shown in (1) shows the I-V characteristics for the transistor. According to the first order model the current is 0 when $V_{GS} \leq V_t$ and it increases linearly when V_{DS} is increased or decreased. We get ^a two points in the regions. These points are saturation points. We get a saturation point for a positive V_{DS} and a negative V_{DS} . When V_{DS} is positive that is 1 we get I_{DS} of 2150126.5 and when V_{DS} is negative ^{that is -0.5} we get I_{DS} of 8600506.

When V_{DS} increases I_{DS} also increases linearly. but at a point $V_{DS} = V_{DSsat}$ happen that point is called saturation point. These two points are given in (1). After this point increasing V_{DS} won't have any effect on I_{DS} , I_{DS} will remain same cause it has reached the saturation point.

~~Same goes for decreasing the V_{DS} .~~