 


Answer to the Q No. 1

For 2 input ~~NAND~~ NAND:

~~There would~~




$$\therefore C_m = 2 + 2 = 4$$

$$\therefore g = \frac{4}{2+1} = \frac{4}{3}$$




For 3 input NAND

 

$$C_m = 2 + 3 = 5$$

$$g = \frac{5}{3}$$

for 4 input NAND:

 

$$\begin{array}{r}
 A \rightarrow 1 \times 4 = 4 \\
 B \rightarrow 1 \times 4 = 4 \\
 C \rightarrow 1 \times 4 = 4 \\
 D \rightarrow 1 \times 4 = 4 \\
 \hline
 16
 \end{array}$$

$$C_{in} = \frac{2+4}{3} = \frac{6}{3} = 2$$

$$g = \frac{6}{3}$$

From these three scenarios we can formulate a common equation for calculating effort for n input NAND.

$$\text{Effort, } g = \frac{n+2}{3}$$

Ans.

Answer to the Q.No. 2

The logical effort ^{of the} inverter is $g=1$, electrical effort of the inverter is $h=1$, The parasitic delay of the inverter is $p_d=1$. So the delay of each stage is, $d = gh + p = 1 + 1 = 2$

The N stage ring oscillator has a period of $2N$ stage delay because of. Therefore total delay of the N stage oscillator would be $2 \times 2N = 4N$.

Here,

$$N = 12$$

$$\therefore \text{delay} = 4 \times 12 = 48$$